

DEVICE MODELLING LAB

Assignment-09

Q1. Simulate the edge triggering D-Flip Flop?

Q2. Simulate the negative-level triggering D-Flip Flop?

Q3. Simulate T-Flip Flop Using NGSPICE?